

## Lab 7: Using RAM

Wednesday, November 06, 2024 2:55 PM

Jack Burton

**TAs:** Cory and Karen


**Summary:** Uses iCE40's built-in RAM to create a visual loopier which records a sequence of LEDs and then repeatedly plays it back from memory.

Bench: 11

### Lab Journal

#### L1

Using two channels:

 

#### L2

I will sample 256 times per second, and the recording duration will be 8 seconds. This is a total of  $256 * 8 = 2048$  samples, so I will need 2048 bits.

### Instantiating Memory

#### L3

Created project on Lattice, added ramdp.vhd to the project, and then instantiated it as a submodule within top.vhd.

### Counter

#### L4

1. Added HSOSC as a component to top.vhd just like in lab 6
2. Built 2-bit fastcounter module, which rolls over after 2 bits reach 11. This will roll over for each 2-bit loopier sample.
3. Built second counter using provided code within top module, and a signal sample\_counter.

### Wiring Everything Up

#### L5

Connected each button to 5V, and then:

1. Connected the record button to a read\_write input (std\_logic)
2. Connected the two writing buttons to a write\_value input (2-bit unsigned)
3. Connected LEDs (through 4.7k ohm resistors) to read\_value output (2-bit unsigned)

After *much* troubleshooting, I realized I hadn't actually grounded the push-buttons.. But after grounding them, the LEDs were correctly playing back the recorded LED input.

#### L6

I added a signal to store the previous value of the record button, at the end of the if rising\_clock. Then I added the conditional logic, which essentially just checked if the previous value and the current value differed. If either of those conditions was met, the sample counter was reset to 0. This successfully caused immediate replay.

## L7

I added another signal to hold the sample\_counter's saved value, and placed this in the conditional for when the record button is released. This should save the sample\_counter's position when the record button is released


Then, within this same conditional, I added another conditional which checks if sample\_counter reaches 0 (so if it reaches the end of the recording/sample size). Then this sets sample\_counter to the sample\_counter saved value signal, to loop back to the recording rather than continuing to iterate through the whole RAM.

This successfully works and allows me to record any length pattern and watch it playback endlessly.

**Video of circuit working (recording a small sample and then replaying it—my sample time is just large that's why there is the**

**delay):** [https://drive.google.com/file/d/1AsiDn3Wka3SxJyyThhfPDm7\\_93RfrgkZ/view?usp=sharing](https://drive.google.com/file/d/1AsiDn3Wka3SxJyyThhfPDm7_93RfrgkZ/view?usp=sharing)

### Completed Circuit:

 

## VHDL Code

(ramdp.vhd was unmodified from the provided file)

### Top.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;

entity top is
port (
  read_write : in std_logic; -- pin 2
  write_value : in std_logic_vector(1 downto 0); -- pins 3 and 4
  read_value : out std_logic_vector(1 downto 0) -- pins 28 and 38
);
end top;

architecture synth of top is
  component ramdp is
    generic (
      WORD_SIZE : natural := 2; -- Bits per word (read/write block size)
      N_WORDS : natural := 64; -- Number of words in the memory
      ADDR_WIDTH : natural := 6 -- This should be log2 of N_WORDS; see the Big Guide to Memory for a way to eliminate this manual calculation
    );
    port (
      clk : in std_logic;
      r_addr : in std_logic_vector(ADDR_WIDTH - 1 downto 0);
```

```

    r_data : out std_logic_vector(WORD_SIZE - 1 downto 0);
    w_addr : in std_logic_vector(ADDR_WIDTH - 1 downto 0);
    w_data : in std_logic_vector(WORD_SIZE - 1 downto 0);
    w_enable : in std_logic
  );
end component;

component HSOSC is
generic (
CLKHF_DIV : String := "0b00");
port (
CLKHFPFU : in std_logic := 'X';
CLKHFEN : in std_logic := 'X';
CLKHF : out std_logic := 'X'
);
end component;

component fastcounter is
port(
clk : in std_logic;
result : out std_logic_vector(22 downto 0)
);
end component;

signal clk : std_logic;
signal sample_counter : unsigned(5 downto 0) := 6d"0";
signal intermediate_counter : std_logic_vector(22 downto 0);
signal read_write_prev : std_logic;
signal sample_counter_saved : unsigned(5 downto 0);
begin
osc : HSOSC generic map ( CLKHF_DIV => "0b00")
port map (CLKHFPFU => '1',
CLKHFEN => '1',
CLKHF => clk);
fc : fastcounter port map (clk, intermediate_counter);
ram : ramdp port map (clk, w_enable => read_write, w_data =>
write_value, r_addr => std_logic_vector(sample_counter), w_addr =>
std_logic_vector(sample_counter), r_data => read_value);
process(clk) is
begin
if rising_edge(clk) then
if intermediate_counter = 23d"0" then -- Counter just rolled over
sample_counter <= sample_counter + 1;
end if;
-- L6: If record button is pressed or released, reset sample_counter
(for immediate replay)
if (not read_write and read_write_prev) or (read_write and not
read_write_prev) then
sample_counter <= 6d"0";
end if;
read_write_prev <= read_write;
-- L7: Looping over recorded portion, not entire memory
if (read_write and not read_write_prev) then -- control button
released
sample_counter_saved <= sample_counter;
if sample_counter = 6d"0" then
sample_counter <= sample_counter_saved;
end if;
end if;
end if;

```

```
end if;  
end process;  
end;
```

#### Fastcounter.vhd

```
library IEEE;  
use IEEE.std_logic_1164.all;  
use IEEE.numeric_std.all;  
  
entity fastcounter is  
port(  
  clk : in std_logic;  
  result : out std_logic_vector(22 downto 0)  
);  
end fastcounter;  
  
architecture synth of fastcounter is  
  signal count : unsigned(22 downto 0);  
begin  
  process (clk) begin  
    if rising_edge(clk) then  
      count <= count + 1;  
    end if;  
  end process;  
  result <= std_logic_vector(count);  
end;
```